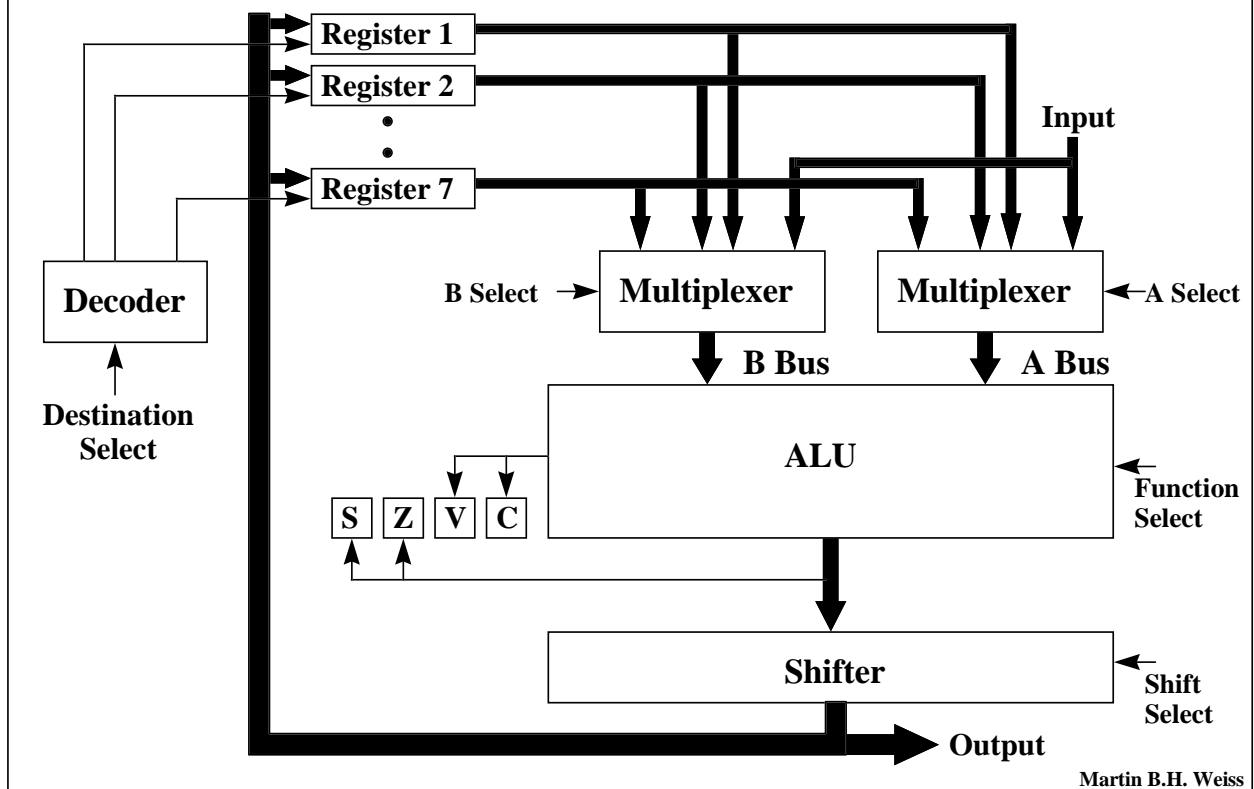


## A Simple Processor Architecture



Martin B.H. Weiss

## ALU

- Performs Arithmetic Functions
- Performs Logic Functions
- Function is Selected by Control
- Status Bits
  - C - Carry
  - V - Overflow
  - Z = 1 If Resultant Contains All Zeros
  - S - Sign Bit of the Result
- Decoder Selects Destination for the Resultant

Martin B.H. Weiss

# ALU

- **Inputs**
  - **Operands**
  - **Input Carry**
  - **Operation Select**
    - **Add**
    - **Subtract**
    - **AND**
    - **OR**
    - **XOR**
  - **Mode (Arithmetic or Logic) Select**
- **Outputs**
  - **Resultant**
  - **Output Carry**

Martin B.H. Weiss

Arithmetic-Logic Unit and Processor Design - 3

University of Pittsburgh

## ALU Function Table

Operation Select				Operation	Function
$S_2$	$S_1$	$S_0$	$C_{in}$		
0	0	0	0	$F=A$	Transfer A
0	0	0	1	$F=A+1$	Increment A
0	0	1	0	$F=A+B$	Add A and B
0	0	1	1	$F=A+B+1$	Add A and B With Carry
0	1	0	0	$F=A+B'$	Add A and One's Complement of B
0	1	0	1	$F=A+B'+1$	Subtract B From A
0	1	1	0	$F=A-1$	Decrement A
0	1	1	1	$F=A$	Transfer A
1	0	0	0	$F=AB$	AND
1	0	1	0	$F=A+B$	OR
1	1	0	0	$F=A \text{ XOR } B$	Exclusive OR
1	1	1	0	$F=A'$	Complement

Martin B.H. Weiss

Arithmetic-Logic Unit and Processor Design - 4


University of Pittsburgh

## ALU Components

- **Arithmetic**
  - **Parallel Add**
  - **One Full Adder per Bit**
  - **Selection Logic**
- **Logic**
  - **Gates**
  - **Multiplexer**


Martin B.H. Weiss

## Circuit for Arithmetic Component

 


Martin B.H. Weiss

## Circuit for Logic Component

 

Martin B.H. Weiss

## Internal Structure of ALU

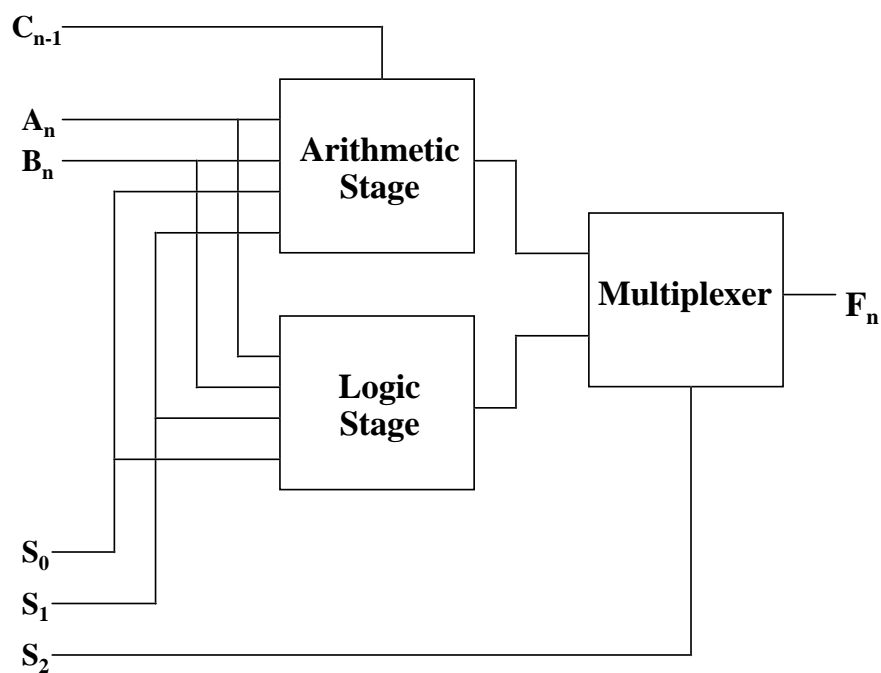

Martin B.H. Weiss

## Shifter

---

- **General**
  - **Extension of Shift Register Circuit is Possible**
  - **This Requires Several Clock Pulses**
  - **This is Time Consuming**
- **Alternate Approach (Figure 7-18, p. 246 of Mano)**
  - **Use Multiplexers**
  - **Wire to Cause Shift Effect**
  - **Control Determines Nature of Shift**
  - **Thus, a Single Clock Cycle is Used**

Martin B.H. Weiss

## Control Unit Requirements


---

- **MUX A Selector**
- **MUX B Selector**
- **ALU Operation Selector**
- **Shift Selector**
- **Destination Selector**

Martin B.H. Weiss
 
## Control Word

- **Number and Organization of Bits Required to Control ALU**
- **Bit Requirements**
  - **A: A Bus Select (Seven Registers Plus Input): 3 bits**
  - **B: B Bus Select (Seven Registers Plus Input): 3 bits**
  - **D: Destination Select (Seven Registers): 3 bits**
  - **F: ALU Control (Four bits)**
  - **H: Shift Control (Three bits)**
  - **TOTAL = 16 bits**
  - **Thus, 16 Bits Can Be Used to Perform All Microoperations**



Martin B.H. Weiss

## Control Word Encoding

Code	Operation (F)		A	B	D	H
	$C_{in} = 0$	$C_{in} = 1$				
0 0 0	$F=A$	$F=A+1$	Input	Input	None	No Shift
0 0 1	$F=A+B$	$F=A+B+1$	R1	R1	R1	SHL
0 1 0	$F=A+B'$	$F=A+B'+1$	R2	R2	R2	SHR
0 1 1	$F=A-1$	$F=A$	R3	R3	R3	Bus=0
1 0 0	$F=AB$		R4	R4	R4	
1 0 1	$F=A+B$		R5	R5	R5	ROL
1 1 0	$F=A \text{ XOR } B$		R6	R6	R6	ROR
1 1 1	$F=A'$		R7	R7	R7	

Martin B.H. Weiss

## Microoperations and Microprograms

---

- **Example Microoperation**
  - $R1 \leftarrow R2 - R3$
  - Symbolically: R2,R3,R1,F=A-B,No Shift
  - Control Word = 010 011 001 0101 000 = 4CA8 (H)
- **Clearly, Many Microoperations Are Possible**
- **Control Memory**
  - Location of Available Microoperations
  - Width of Control Memory = Control Word
- **Microprograms Can be Written Using a Sequence of Microoperations**